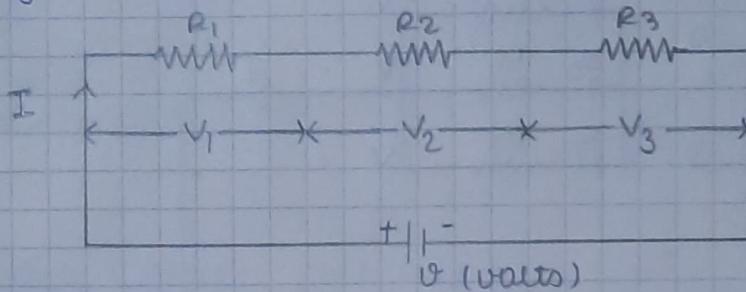




## (1) # Series Equivalent Resistance

~ let us consider a circuit with three resistors of resistance ( $R_1, R_2, R_3$ ) and a voltage source ( $V$ ) which are connected in series.



As we know that voltage gets divided in series connection & current stays the same

$$\therefore V = V_1 + V_2 + V_3 \quad \text{--- (1)}$$

According to Ohm's law, ( $V=IR$ )

$$V_1 = IR_1, V_2 = IR_2, V_3 = IR_3$$

Now put the value of  $V_1, V_2, V_3$  in eq (1)

$$\therefore V = IR_1 + IR_2 + IR_3$$

$$\therefore V = I(R_1 + R_2 + R_3)$$

Also, we know that  $V_{eq} = I R_{eq}$


$$\therefore I R_{eq} = I(R_1 + R_2 + R_3)$$

$$\therefore R_{eq} = R_1 + R_2 + R_3 \quad \checkmark$$

\* Here individual resistance is always less than the equivalent resistance
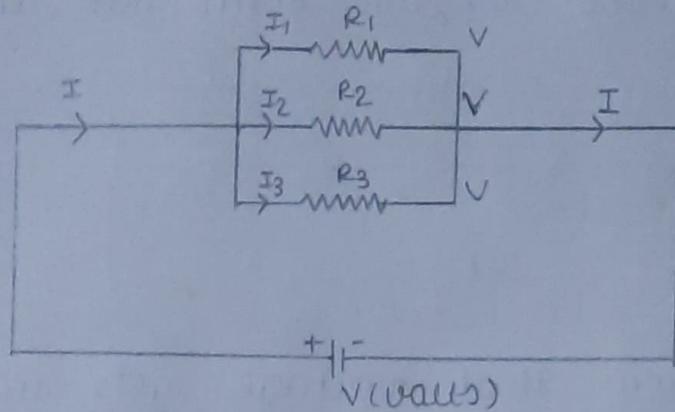
## ~~Part~~ Parallel Equivalent Resistance.

Let us consider a circuit with three resistors of resistance ( $R_1, R_2, R_3$ ) and a voltage source ( $V$ ) which are connected in parallel.



As we know that current gets divided in parallel connection and voltage stays the same.

$$\therefore I = I_1 + I_2 + I_3 \quad \text{--- (1)}$$

According to Ohm's law,  $(V=IR) \Rightarrow (I=\frac{V}{R})$

$$\therefore I_1 = \frac{V}{R_1}, \quad I_2 = \frac{V}{R_2}, \quad I_3 = \frac{V}{R_3}$$

Now put the value of  $I_1, I_2, I_3$  in eq (1).

$$\therefore I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\therefore I = V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

Also, we know that  $I_{eq} = \frac{V}{R_{eq}}$




$$\therefore \frac{V}{R_{eq}} = V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\boxed{\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \quad \checkmark$$

Here, the individual resistance will be more than the equivalent resistance.




#(3) Delta. to Star.

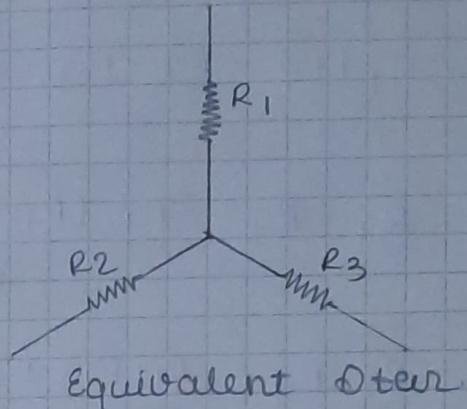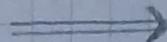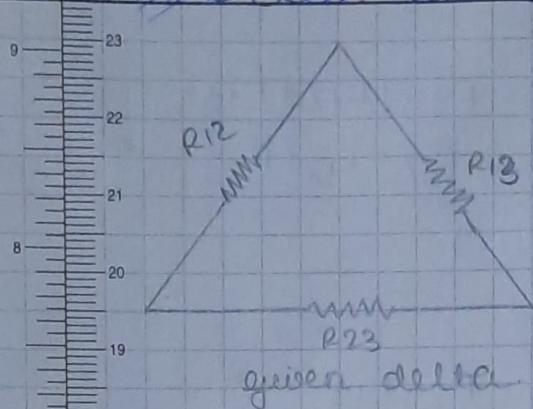

~ Consider three resistances  $R_{12}$ ,  $R_{23}$ ,  $R_{13}$  connected in delta.

Now equivalent resistance b/w A and B

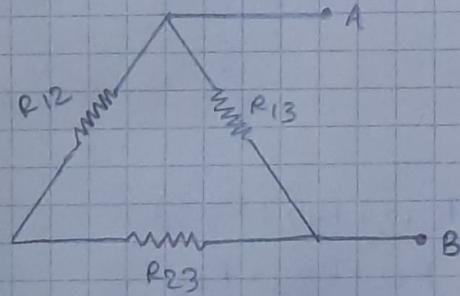


Here,  $R_{13}$  is parallel with  $(R_{12} + R_{23})$

$$R_{13} = \frac{R_{13}(R_{12} + R_{23})}{R_{13} + R_{12} + R_{23}} \quad \text{--- (1)}$$

Similarly,

$$R_{12} = \frac{R_{12}(R_{13} + R_{23})}{R_{12} + R_{13} + R_{23}} \quad \text{--- (2)} \quad \text{&} \quad R_{23} = \frac{R_{23}(R_{12} + R_{13})}{R_{23} + R_{12} + R_{13}} \quad \text{--- (3)}$$

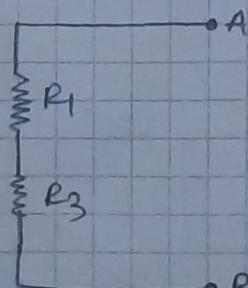Now consider same two terminals of equivalent star - connection



Between A and B resistance  
 $= R_1 + R_3 \quad \text{--- (4)}$

$$\text{Now Comparing eq (1) & (4)} \\ R_1 + R_3 = \frac{R_{13}(R_{12} + R_{23})}{R_{13} + R_{12} + R_{23}} \quad \text{--- (5)}$$

$$R_1 + R_3 = \frac{R_{12}(R_{13} + R_{23})}{R_{12} + R_{13} + R_{23}} \quad \text{--- (6)}$$

$$R_2 + R_3 = \frac{R_{23}(R_{12} + R_{13})}{R_{23} + R_{12} + R_{13}} \quad \text{--- (7)}$$

Now, subtract eq ⑦ from eq ⑥

$$\therefore R_1 + R_2 - R_2 - R_3 = \frac{R_{12}(R_{13} + R_{23})}{R_{12} + R_{13} + R_{23}} - \frac{R_{23}(R_{12} + R_{13})}{R_{12} + R_{13} + R_{23}}$$

$$\therefore R_1 - R_3 = \frac{R_{12}(R_{13} + R_{23}) - R_{23}(R_{12} + R_{13})}{R_{12} + R_{23} + R_{13}}$$

$$\therefore R_1 - R_3 = \frac{R_{12}R_{13} + R_{12}R_{23} - R_{23}R_{12} - R_{23}R_{13}}{R_{12} + R_{23} + R_{13}}$$

$$\therefore R_1 - R_3 = \frac{R_{12}R_{13} - R_{23}R_{13}}{R_{12} + R_{23} + R_{13}}$$

$$\therefore R_1 - R_3 = \frac{R_{13}(R_{12} - R_{23})}{R_{12} + R_{23} + R_{13}} \quad \text{--- (8)}$$

Now add eq ⑧ and eq ⑤

$$\therefore R_1 - R_3 + R_1 + R_3 = \frac{R_{13}(R_{12} - R_{23})}{R_{12} + R_{23} + R_{13}} + \frac{R_{13}(R_{12} + R_{23})}{R_{12} + R_{23} + R_{13}}$$

$$\therefore 2R_1 = \frac{R_{13}(R_{12} - R_{23}) + R_{13}(R_{12} + R_{23})}{R_{12} + R_{23} + R_{13}}$$

$$\therefore 2R_1 = \frac{R_{13}R_{12} - R_{13}R_{23} + R_{13}R_{12} + R_{13}R_{23}}{R_{12} + R_{23} + R_{13}}$$



$$\therefore 2R_1 = \frac{2R_{13}R_{12}}{R_{12} + R_{23} + R_{13}} \Rightarrow R_1 = \boxed{\frac{R_{12}R_{13}}{R_{12} + R_{23} + R_{13}}} \quad \checkmark$$

$$R_2 = \boxed{\frac{R_{12}R_{23}}{R_{12} + R_{23} + R_{13}}} \quad \checkmark$$

$$R_3 = \boxed{\frac{R_{13}R_{23}}{R_{12} + R_{23} + R_{13}}} \quad \checkmark$$



## # Star to Delta

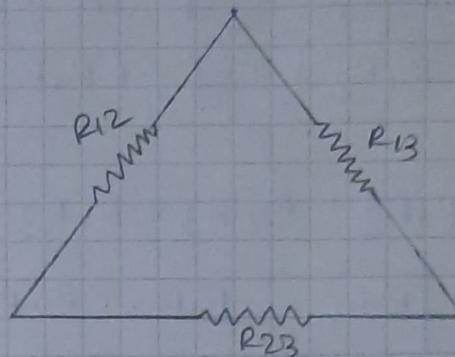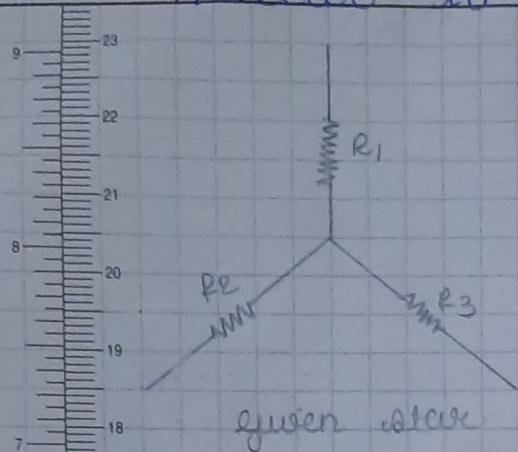

Consider three resistances  $R_1, R_2, R_3$  connected in star.

We know that

$$R_1 = \frac{R_{12} \cdot R_{13}}{R_{12} + R_{23} + R_{13}} \quad \text{--- (1)}$$

$$R_2 = \frac{R_{12} \cdot R_{23}}{R_{12} + R_{23} + R_{13}} \quad \text{--- (2)}$$

$$R_3 = \frac{R_{13} \cdot R_{23}}{R_{12} + R_{23} + R_{13}} \quad \text{--- (3)}$$

Multiply eq (1) & (2)

$$R_1 \cdot R_2 = \frac{(R_{12} \cdot R_{13})(R_{12} \cdot R_{23})}{(R_{12} + R_{23} + R_{13})^2} = \frac{R_{12}^2 \cdot R_{13} \cdot R_{23}}{(R_{12} + R_{23} + R_{13})^2} \quad \text{--- (4)}$$

$$\text{Similarly, } R_2 \cdot R_3 = \frac{R_{23}^2 \cdot R_{12} \cdot R_{13}}{(R_{12} + R_{23} + R_{13})^2} \quad \text{--- (5)}$$

$$R_3 \cdot R_1 = \frac{R_{13}^2 \cdot R_{12} \cdot R_{23}}{(R_{12} + R_{23} + R_{13})^2} \quad \text{--- (6)}$$

Add eq (4), (5) & (6).

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_{12}^2 R_{13} R_{23} + R_{23}^2 R_{12} R_{13} + R_{13}^2 R_{12} R_{23}}{(R_{12} + R_{23} + R_{13})^2}$$

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_{12} R_{13} R_{23} (R_{12} + R_{23} + R_{13})}{(R_{12} + R_{23} + R_{13})(R_{12} + R_{23} + R_{13})}$$

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_{12} R_{13} R_{23}}{R_{12} + R_{23} + R_{13}} \quad \text{--- (7)}$$

Substitute eq ① in eq ⑦

$$\therefore R_1 R_2 + R_2 R_3 + R_1 R_3 = \frac{R_{12} R_{13}}{R_2 + R_{23} + R_{13}} (R_{23})$$

$$\therefore R_1 R_2 + R_2 R_3 + R_1 R_3 = R_1 \cdot R_{23}$$

$$\therefore R_{23} = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1} \quad \checkmark$$

$$\therefore R_{12} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} \quad \checkmark$$

$$\therefore R_{13} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} \quad \checkmark$$

# Temperature Co-efficient of Resistance.

~ let  $R_0$  be the resistance at  $0^\circ\text{C}$   
resistance at  $T^\circ\text{C}$  then change  
is directly proportional to,

i) The original resistance.

$$\Delta R \propto R_0 \quad \text{--- ①}$$

ii) The change in temperature

$$\Delta R \propto \Delta T \quad \text{--- ②}$$


Combining Comparing eq ① & ②.

$$\Delta R \propto R_0 \Delta T$$

$$\therefore \Delta R = \alpha \cdot R_0 \Delta T$$

$$\therefore \alpha = \frac{\Delta R}{R_0 \Delta T} \cdot \text{C}^{-1} / \text{K}^{-1}.$$

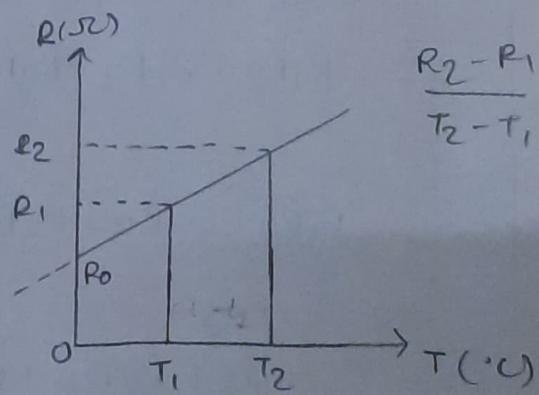
\*  $\frac{\Delta R}{\Delta T}$  slope of the graph.




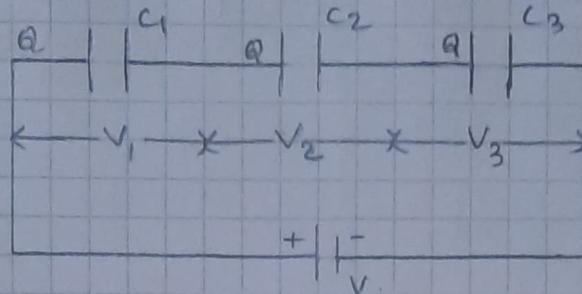
## # Series Equivalent Capacitance.

~ let us consider a circuit with three capacitors with capacitance  $C_1, C_2, C_3$  and a voltage source ( $V$ ) connected in series.



~ As we know that current stays same in series connection so the charge on each capacitor is also same but potential difference is different across each capacitor.

$$V = V_1 + V_2 + V_3 \quad \text{--- (1)}$$

But we know that ( $Q = CV$ )  $\Rightarrow (V = \frac{Q}{C})$

$$\therefore V_1 = \frac{Q}{C_1}, \quad V_2 = \frac{Q}{C_2}, \quad V_3 = \frac{Q}{C_3}$$

Put the value of  $V_1, V_2$  and  $V_3$  in eq (1)

$$V = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$$

$$\therefore V = Q \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$


Also, we know that  $V_{eq} = \frac{Q}{C_{eq}}$

$$\therefore \frac{Q}{C_{eq}} = Q \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$

$$\therefore \boxed{\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}} \quad \checkmark$$
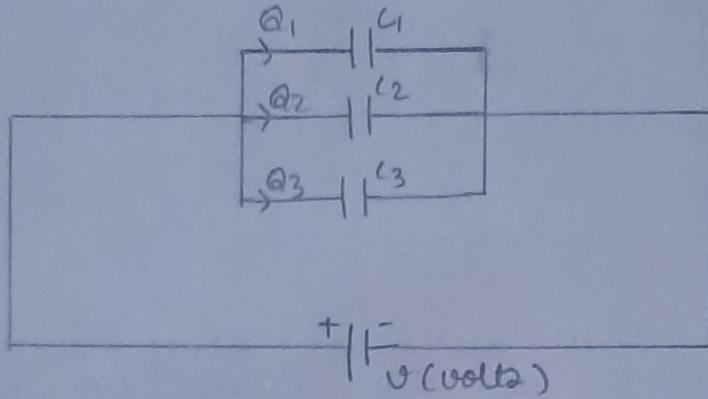
## # Parallel Equivalent Capacitance

Let us consider a circuit with three capacitor with capacitance of  $C_1, C_2, C_3$  and a voltage source  $V$  are connected in parallel.



As we know that in parallel connection potential difference stays the same but current is different  
so charge across all the capacitor is different

$$Q = Q_1 + Q_2 + Q_3 \quad \text{--- (1)}$$

But we know that, ( $Q = CV$ )

$$\therefore Q_1 = C_1 V, Q_2 = C_2 V, Q_3 = C_3 V$$

Put the value of  $Q_1, Q_2, Q_3$  in eq (1).

$$\therefore Q = C_1 V + C_2 V + C_3 V$$

$$\therefore Q = V(C_1 + C_2 + C_3)$$

Also, we know that  $Q_{eq} = C_{eq} \cdot V$ .

$$\therefore C_{eq} V = V(C_1 + C_2 + C_3)$$

$$\therefore \boxed{C_{eq} = C_1 + C_2 + C_3} \checkmark$$

## # Uniform Dielectric Medium

Consider a capacitor having two parallel plate of area  $A \text{ m}^2$  separated by a dielectric medium of thickness  $d$  meters with relative permittivity  $\epsilon_r$ .

$$\therefore \text{Electric flux density}, \quad \Theta = \frac{Q}{A} \quad \text{--- (1)}$$

$$\text{Electric field intensity}, \quad E = \frac{V}{d} \quad \text{--- (2)}$$

Here, Electric flux density can also be defined as,

$$\Theta = \epsilon E$$

$$\therefore \frac{Q}{A} = \epsilon \frac{V}{d} \quad (\text{From eq (1) \& (2)})$$


$$\therefore \frac{Q}{V} = \epsilon \frac{A}{d}$$

$$\therefore C = \epsilon \frac{A}{d} \quad (\because \frac{Q}{V} = C) \quad (\epsilon = \epsilon_0 \epsilon_r)$$

$$\therefore \boxed{C = \frac{\epsilon_0 \epsilon_r A}{d}} \quad 'F' \text{ (Farad)}$$
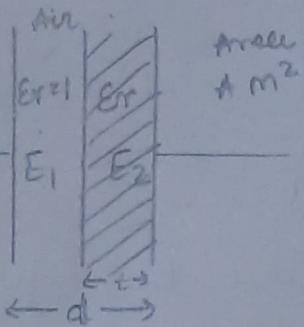
## # Medium Partly Air.

~ Here, the medium consists partly air and partly dielectric slab of thickness  $t$  with relative permittivity  $\epsilon_r$ .



We know that,  $\Theta = \epsilon E$

$$\therefore E_1 = \frac{\Theta}{\epsilon_0} \text{ for air}$$

$$\therefore E_2 = \frac{\Theta}{\epsilon_0 \epsilon_r} \text{ for medium}$$

~ Potential difference between plates is,

$$V = V_1 + V_2$$

$$\therefore V = E_1(d-t) + E_2 t \quad (\because E = \frac{V}{d} \Rightarrow V = Ed)$$

$$\therefore V = \frac{\Theta}{\epsilon_0}(d-t) + \frac{\Theta}{\epsilon_0 \epsilon_r}(t)$$

$$\therefore V = \frac{\Theta}{\epsilon_0} \left[ (d-t) + \frac{t}{\epsilon_r} \right]$$

$$\therefore \text{But } \Theta = \frac{Q}{A}$$

$$\therefore V = \frac{Q}{A \epsilon_0} \left[ d - \left( t - \frac{t}{\epsilon_r} \right) \right]$$

$$\therefore A \epsilon_0 = \frac{Q}{V} \left[ d - \left( t - \frac{t}{\epsilon_r} \right) \right]$$

$$\text{But } C = \frac{Q}{V}$$


$$\therefore A \epsilon_0 = C \left[ d - \left( t - \frac{t}{\epsilon_r} \right) \right]$$

$$\therefore \boxed{C = \frac{\epsilon_0 A}{\left[ d - \left( t - \frac{t}{\epsilon_r} \right) \right]} F} \checkmark$$


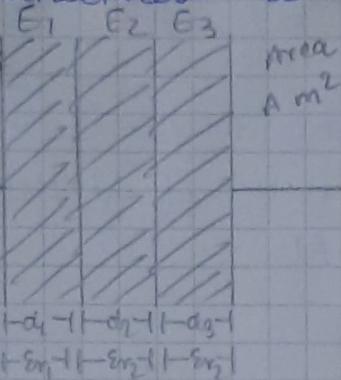
## # Composite Medium

~ Here, there are three composite medium with thickness  $d$  and relative permittivity  $\epsilon_r$ .



We know that,  $\sigma = \epsilon E$

$$\therefore E_1 = \frac{\sigma}{\epsilon_0 \epsilon_{r1}}$$

$$\therefore E_2 = \frac{\sigma}{\epsilon_0 \epsilon_{r2}}$$

$$\therefore E_3 = \frac{\sigma}{\epsilon_0 \epsilon_{r3}}$$

~ Potential difference b/w plates is,

$$V = V_1 + V_2 + V_3$$

$$\text{But } E = \frac{V}{D} \Rightarrow V = E \cdot D.$$

$$\therefore V = E_1 d_1 + E_2 d_2 + E_3 d_3$$

$$\therefore V = \frac{\sigma}{\epsilon_0 \epsilon_{r1}} \cdot d_1 + \frac{\sigma}{\epsilon_0 \epsilon_{r2}} \cdot d_2 + \frac{\sigma}{\epsilon_0 \epsilon_{r3}} \cdot d_3$$

$$\therefore V = \frac{\sigma}{\epsilon_0} \left[ \frac{d_1}{\epsilon_{r1}} + \frac{d_2}{\epsilon_{r2}} + \frac{d_3}{\epsilon_{r3}} \right]$$

$$\text{Also, } \sigma = \frac{Q}{A}$$

$$\therefore V = \frac{Q}{A \epsilon_0} \left[ \frac{d_1}{\epsilon_{r1}} + \frac{d_2}{\epsilon_{r2}} + \frac{d_3}{\epsilon_{r3}} \right]$$


$$\therefore \epsilon_0 A = \frac{Q}{V} \left[ \frac{d_1}{\epsilon_{r1}} + \frac{d_2}{\epsilon_{r2}} + \frac{d_3}{\epsilon_{r3}} \right]$$

$$\text{But, } C = \frac{Q}{V}$$

$$\therefore C = \frac{\epsilon_0 A}{\left[ \frac{d_1}{\epsilon_{r1}} + \frac{d_2}{\epsilon_{r2}} + \frac{d_3}{\epsilon_{r3}} \right]} \quad \checkmark$$
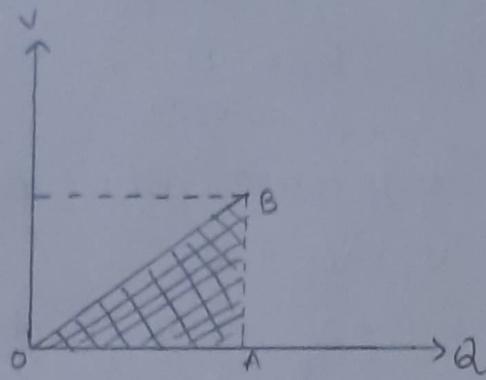
## # Energy Stored in Capacitor

- When an uncharged capacitor is connected to D.C. supply, the voltage across it rises gradually & it starts storing energy.
- The energy required to charge the capacitor with  $Q$  coulombs at a potential difference of  $V$  volts is given by the area of triangle OAB.



∴ Energy stored in a capacitor = Area of  $\triangle OAB$

$$\therefore E = \frac{1}{2} \times OA \times AB$$

$$\therefore E = \frac{1}{2} \times Q \times V$$

$$\therefore E = \frac{1}{2} \times (CV) \times V \quad [\because Q = CV]$$

$$\therefore \boxed{E = \frac{1}{2} \times C \times V^2} \quad \text{Joule (J)}$$

OR


$$\therefore E = \frac{1}{2} \times C \times \frac{Q^2}{C^2}$$

$$\therefore E = \frac{1}{2} \times \frac{Q^2}{C} \text{ Joule}$$


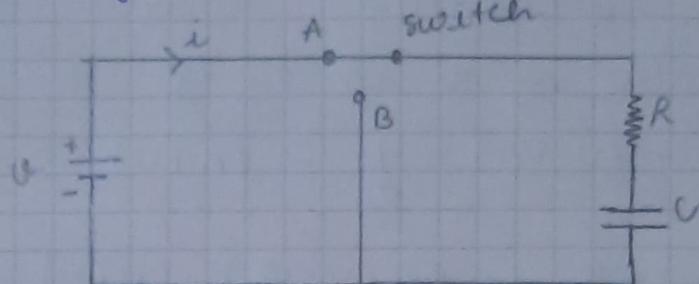
## # Charging of a Capacitor

Consider a circuit consisting of a resistor, and a capacitor connected in series with a switch A and battery of  $V$  volts. Current is flowing through the circuit <sup>through</sup> switch A.



At any instant during charging,  
 $V_C$  = Potential difference across capacitor.

$i$  = charging current

$$i = \frac{dq}{dt} = \frac{d(C \cdot V_C)}{dt} \quad (\because Q = C \cdot V_C)$$

According to KVL,

$$V = V_C + V_R \quad \text{--- (1)}$$

$$\therefore V = V_C + iR$$

$$\therefore V = V_C + R \cdot \frac{d(C \cdot V_C)}{dt}$$

$$\therefore V = V_C + RC \cdot \frac{dV_C}{dt}$$

$$\therefore \frac{dV_C}{V - V_C} = \frac{dt}{RC} \quad \text{--- (2)}$$

Integrating both sides

$$\int \frac{dV_C}{V - V_C} = \int \frac{dt}{RC} + K ; K \text{ is constant of integration}$$

$$\therefore \frac{-1}{V - V_C} = \frac{t}{RC} + K$$

$$- \ln(V - V_C) = \frac{t}{RC} + K \quad \text{--- (3)}$$

At the instant of closing the switch.

$$t=0, V_C=0$$

$$\therefore -\ln(V) = 0 + K$$

$$\therefore K = -\ln(V)$$


put the value of K in eq ③

$$-\ln(V-V_C) = \frac{-t}{RC} - \ln(V)$$

$$\therefore \frac{-t}{RC} = \ln(V-V_C) - \ln(V)$$

$$\therefore e^{-t/RC} = \frac{V-V_C}{V}$$
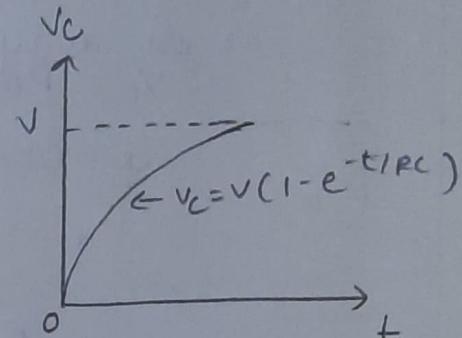
$$\therefore \boxed{V_C = V(1 - e^{-t/RC})} \quad \textcircled{3}$$



similarly at any instant

$$V_C = \frac{Q}{C}$$

$$\therefore \frac{Q}{C} = \frac{Q}{C} (1 - e^{-t/RC})$$

$$\therefore \text{Now, } V - V_C = \frac{V}{R} i R$$

$$\therefore i = \frac{V - V_C}{R}$$

$$\therefore i = \frac{V - \cancel{\frac{V e^{-t/RC}}{R}}}{R} i = \frac{V e^{-t/RC}}{R}$$


$$\therefore i = \frac{V}{R} e^{-t/RC}$$

[ $\because$  initial charging]  
current =  $\frac{V}{R}$   
(I<sub>0</sub>)

$$\therefore \boxed{i = I_0 e^{-t/RC}} \quad \textcircled{4}$$
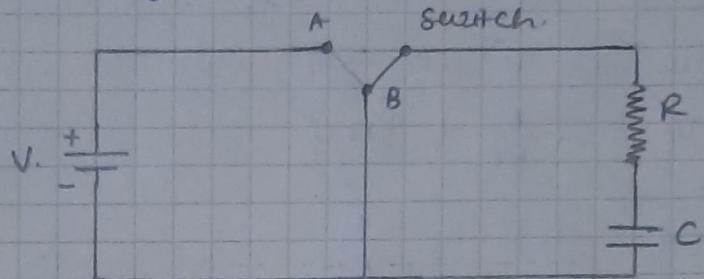
## # Discharging of a Capacitor

Consider a circuit consisting of a resistor, and a capacitor connected in series with a switch B and battery of  $V$  volts. Current is flowing through the circuit through switch B.



At any instant during discharging,  
 $V_C = \text{PD across capacitor}$

$i$  = discharging current

$$\therefore i = \frac{dq}{dt} = \frac{d(C \cdot V_C)}{dt} \quad [ \because Q = C \cdot V_C ]$$

According to KVL,

$$0 = V_G + V_R \quad \text{--- (1)}$$

$$\therefore 0 = V_G + iR$$

$$\therefore 0 = V_G + R \cdot \frac{dq}{dt} \quad \cancel{[ \because Q = C \cdot V_C ]}$$


$$\therefore 0 = V_G + RC \cdot \frac{dV_C}{dt}$$

$$\therefore \frac{dV_C}{V_C} = -\frac{dt}{RC} \quad \text{--- (2)}$$

Integrating both sides

$$\int \frac{dV_C}{V_C} = - \int \frac{dt}{RC} + K$$
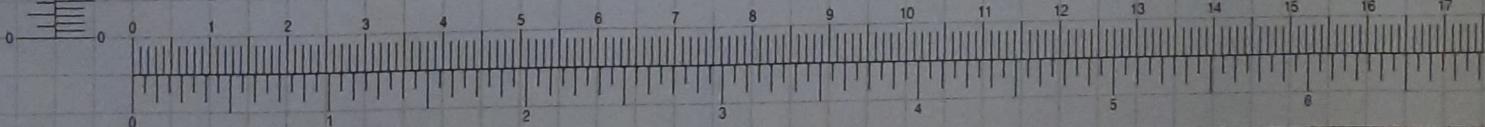
$$\therefore \ln V_C = -\frac{t}{RC} + K \quad \text{--- (3)}$$



→ at the instant of closing the switch,  
 $t=0 \quad V_C = V$


$$\ln(V) = 0 + K \\ \therefore K = \ln V.$$

Put the value of  $K$  in eq (3).

$$\ln V_C = -\frac{t}{RC} + \ln V.$$

$$\therefore \ln V_C - \ln V = -\frac{t}{RC}$$
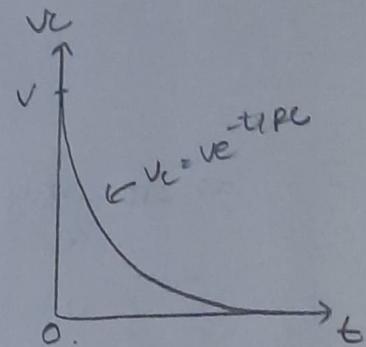
$$\therefore \frac{V_C - V}{V} = e^{-t/RC} \\ \therefore [V_C = V e^{-t/RC}]$$



Similarly at any instant,

$$V_C = \frac{Q}{C}$$

$$\therefore \frac{Q}{C} = \frac{Q}{C} e^{-t/RC}$$

$$\text{Now, } i = -\frac{V_R}{R}$$

$$\therefore V_R = V_C$$

$$\therefore i = -\frac{V_C}{R}$$

$$\therefore i = -\frac{V}{R} e^{-t/RC}$$

$$\therefore [i = -I_0 e^{-t/RC}]$$

[ $-I_0$  = initial discharge current]

$$-I_0 = -\frac{V_R}{R}$$


Q.1

Explain series and parallel magnetic circuit.

→ Series Magnetic Circuit

A magnetic circuit which has only one path for the flux is known as series magnetic circuit.

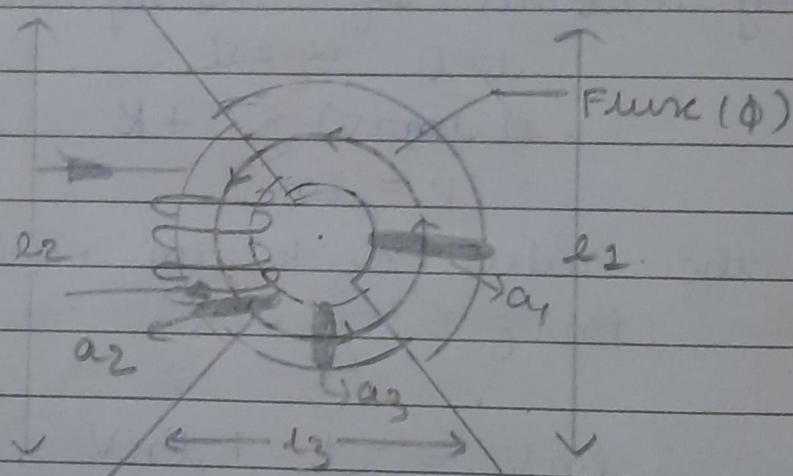- Let coil wound on ring has  $N$  turns carrying a current of  $I$  amperes.



The total reluctance of the magnetic circuit,

$$S_T = S_1 + S_2 + S_3 \\ = \frac{l_1}{\mu_1 a_1} + \frac{l_2}{\mu_2 a_2} + \frac{l_3}{\mu_3 a_3}$$

Here, since MMF is different same as potential difference in series electric circuit

$$\Phi_T = \frac{(MMF)_T}{S_T} = \frac{(NI)_T}{S_T} = \frac{NI}{S_1 + S_2 + S_3}$$


$$\therefore NI = \Phi_T (S_1 + S_2 + S_3)$$

$$\therefore NI = S_1 \phi + S_2 \phi + S_3 \phi$$

$$\therefore (MMF)_T = (MMF)_1 + (MMF)_2 + (MMF)_3$$
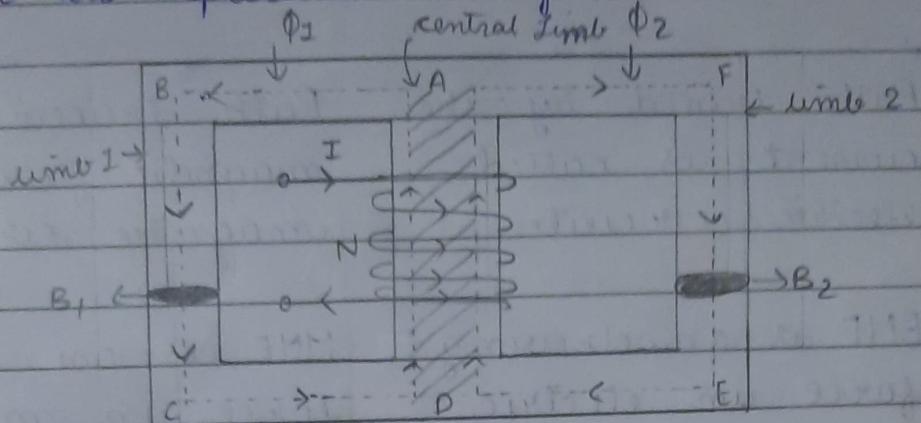
## Parallel Magnetic Circuit

A magnetic circuit which has more than one path for the flux is known as parallel magnetic circuit.



$$\text{Flux} = \frac{\text{MMF}}{\text{reluctance}}$$

$$\therefore \text{MMF} = \Phi \times S$$

$$\text{For path ABCDA, } NI = \Phi_1 S_1 + \Phi c S_c$$

$$\text{For path AFEDA, } NI = \Phi_2 S_2 + \Phi c S_c$$

$$\text{Here, } S_1 = \frac{l_1}{4a_1}, S_2 = \frac{l_2}{4a_2}, S_c = \frac{l_c}{4a_c}$$

$a_1 = a_2 = a_c$  = area of cross-section

$\therefore \text{Total MMF} = \text{MMF required by central limb} + \text{MMF required by any one of outer limbs}$

$$\therefore (NI)_T = (NI)_{AD} + (NI)_{ABCD} / (NI)_{AFED}$$

$$\text{also, } \Phi_1 S_1 = \Phi_2 S_2$$



## # Efficiency.

i) Half-wave Rectifier

$$\eta = \frac{P_{dc}}{P_{ac}} \times 100\%$$

we know that,

$$P_{dc} = I_{dc}^2 R_L \quad \& \quad P_{ac} = I_{rms}^2 (R_L + r_f)$$

$$\therefore \eta = \frac{I_{dc}^2 R_L}{I_{rms}^2 (R_L + r_f)} \times 100\%$$

$$\text{Also, } I_{dc} = \frac{I_m}{\pi} \quad I_{rms} = \frac{I_m}{2}$$

$$\therefore \eta = \frac{\left(\frac{I_m}{\pi}\right)^2 R_L}{\left(\frac{I_m}{2}\right)^2 (R_L + r_f)} \times 100\%$$

$$\therefore \eta = \frac{4 I_m^2 R_L}{\pi^2 I_m^2 (R_L + r_f)} \times 100\%$$

$$\therefore \eta = \frac{4}{9.85} \times \frac{R_L}{R_L + r_f} \times 100\%$$

$$\therefore \eta = \frac{0.406 R_L}{R_L + r_f} \times 100\%$$

$$\therefore \eta = \frac{0.406}{1 + \frac{r_f}{R_L}} \times 100\%$$

\* Here we see here the efficiency will be maximum if  $r_f$  is negligible as compared to  $R_L$ .

$$\boxed{\eta = 40.6\%}$$

### iii) Full-wave Rectifier

$$\eta = \frac{P_{dc}}{P_{ac}} \times 100\%$$

We know that,

$$P_{dc} = I_{dc}^2 R_L$$

$$P_{ac} = I_{rms}^2 (R_L + r_f)$$

$$\therefore \eta = \frac{I_{dc}^2 R_L}{I_{rms}^2 (R_L + r_f)} \times 100\%$$

$$\text{But } I_{dc} = \frac{2Im}{\pi} \quad \& \quad I_{rms} = \frac{Im}{\sqrt{2}}$$

$$\therefore \eta = \frac{\left(\frac{2Im}{\pi}\right)^2 R_L}{\left(\frac{Im}{\sqrt{2}}\right)^2 (R_L + r_f)} \times 100\%$$

$$\therefore \eta = \frac{4Im^2 \times 2}{\pi^2 Im^2} \times \frac{(R_L)}{(R_L + r_f)} \times 100\%$$

$$\therefore \eta = \frac{8}{\pi^2} \times \frac{R_L}{R_L + r_f} \times 100\%$$

$$\therefore \eta = \frac{8}{9.85} \times \frac{R_L}{R_L + r_f} \times 100\%$$

$$\therefore \eta = \frac{0.812 R_L}{R_L + r_f} \times 100\%$$

$$\therefore \eta = \frac{0.812}{1 + \frac{r_f}{R_L}} \times 100\%$$

\* Here, the efficiency will be max. if we neglect  $r_f$  as compared to  $R_L$

$$\therefore \boxed{\eta = 81.2\%}$$

## # Ripple Factor.

ii) Half - Wave Rectifier

$$I_{rms} = \sqrt{I_{dc}^2 + I_{ac}^2}$$

$$\therefore I_{ac} = \sqrt{I_{rms}^2 - I_{dc}^2}$$

Now divide both side by  $I_{dc}$ .

$$\therefore \frac{I_{ac}}{I_{dc}} = \frac{1}{I_{dc}} (\sqrt{I_{rms}^2 - I_{dc}^2})$$

$$\therefore Y = \frac{1}{I_{dc}} (\sqrt{I_{rms}^2 - I_{dc}^2})$$

$\left[ \because \frac{I_{ac}}{I_{dc}} = \text{Ripple Factor} \right]$

$$\therefore Y = \sqrt{\frac{I_{rms}^2 - I_{dc}^2}{I_{dc}^2}}$$

$$\therefore Y = \sqrt{\left(\frac{I_{rms}^2}{I_{dc}^2}\right)} - 1$$

$$\text{But, } I_{rms} = \frac{I_m}{2} \quad \& \quad I_{dc} = \frac{I_m}{\pi}$$

$$\therefore Y = \sqrt{\left(\frac{\frac{I_m^2}{4}}{\frac{I_m^2}{\pi^2}}\right)} - 1$$

$$\therefore Y = \sqrt{\left(\frac{\pi^2}{4}\right)} - 1$$

$$\therefore Y = \sqrt{2.46} - 1$$

$$\therefore Y = \sqrt{1.46}$$

$$\boxed{\therefore Y = 1.21} \checkmark$$

ii) Full-Wave Rectifier

$$I_{\text{rms}}^2 = \sqrt{I_{\text{dc}}^2 + I_{\text{ac}}^2}$$

$$\therefore I_{\text{ac}}^2 = \sqrt{I_{\text{rms}}^2 - I_{\text{dc}}^2}$$

Divide by  $I_{\text{dc}}^2$  both sides

$$\therefore \frac{I_{\text{ac}}}{I_{\text{dc}}} = \frac{1}{I_{\text{dc}}} (\sqrt{I_{\text{rms}}^2 - I_{\text{dc}}^2})$$

$\left[ \therefore \frac{I_{\text{ac}}}{I_{\text{dc}}} = \text{Ripple Factor} \right]$

$$\therefore Y = \frac{1}{I_{\text{dc}}} (\sqrt{I_{\text{rms}}^2 - I_{\text{dc}}^2})$$

$$\therefore Y = \sqrt{\frac{I_{\text{rms}}^2 - I_{\text{dc}}^2}{I_{\text{dc}}^2}}$$

$$\therefore Y = \sqrt{\frac{I_{\text{rms}}^2}{I_{\text{dc}}^2} - 1}$$

$$\text{But } I_{\text{rms}} = \frac{I_m}{\sqrt{2}} \quad \& \quad I_{\text{dc}} = \frac{2I_m}{\pi}$$

$$\therefore Y = \sqrt{\left( \frac{\frac{I_m^2}{2}}{\frac{4I_m^2}{\pi^2}} \right) - 1}$$

$$\therefore Y = \sqrt{\left( \frac{\pi^2}{8} \right) - 1}$$

$$\therefore Y = \sqrt{1.23 - 1}$$

$$\therefore Y = \sqrt{0.23}$$

$$\therefore Y = 0.48$$